

Sample Test Paper - I

Course Name : Computer Engineering Group

Course Code : CO/CM/CD/IF/CW

Semester : Third

Subject Title : Digital Techniques

Marks : 25

**17333**

Hours: 1 Hrs.

**Q.1) Attempt any THREE:**

**09 Marks**

- a) Define
  - i) Propagation delay
  - ii) Fan-in
  - iii) Fan-out
- b) Convert the following:
  - i)  $(42)_{10} = (?)_2$
  - ii)  $(67)_8 = (?)_2$
  - iii)  $(1101011)_2 = (?)_H$
- c) Draw the symbol, logical Expression & truth table of the following gates.
  - i) AND gate
  - ii) Ex – OR gate
- d) Design anHalf Adder circuit with truth table, K – map and logical circuit diagram.

**Q. 2) Attempt any TWO:**

**08 Marks**

- a) Compare TTL & CMOS logic families on the basis of
  - i) Propagation delay
  - ii) Fan-in
  - iii) Fan-out
  - iv) Power dissipation.
- b) State and prove De Morgan’s theorem.
- c) Reduce the following Boolean expression using K – map.  
 $Y = \sum m_0, m_2, m_4, m_6, m_8, m_9, m_{10}, m_{12}, m_{13}, m_{14}$   
Draw the logical circuit diagram of the simplified expression using basic gates

**Q.3) Attempt any TWO:**

**08 Marks**

- a) Subtract using 1’s Complement & 2’s complement method.  
 $(110100)_2 - (111000)_2$
- b) Draw the logical circuit diagram of AND, OR, NOT & NOR gates using NAND gates.
- c) Simplify the following Boolean expressions.
  - i)  $Y = \overline{AB} + \overline{A.B} + \overline{BC}$
  - ii)  $Y = AB + B(\overline{B}+C) + \overline{A\overline{B}}$

**Sample Test Paper - II**

**Course Name : Computer Engineering Group**

**Course Code : CO/CM/CD/IF/CW**

**Semester : Third**

**Subject Title : Digital Techniques**

**Marks : 25**

**17333**

**Hours: 1 Hrs.**

---

**Q.1) Attempt any THREE: (3x3)**

**09 Marks**

- a) State the need for multiplexers. Draw the block diagram of 4:1 Mux.
- b) Differentiate between combinational logic & Sequential logic circuits (any 3 points).
- c) Draw a clock signal and explain positive edge triggering & negative edge triggering.
- d) Define the following specifications of A – D convertor
  - i) Quantization noise
  - ii) Conversion Time
  - iii) Resolution

**Q.2) Attempt any TWO: (2x4)**

**08 Marks**

- a) Draw the block diagram of BCD to 7 – segment decoder/ driver and draw its truth table. Give the function of Lamp Test and Ripple Blanking input pins.
- b) What is Race- around condition in JK flip flop and how it can be eliminated?
- c) Draw the logical circuit diagram of 3 – bit ripple counter and draw its timing diagram showing clock and outputs of each flip Hop.

**Q.3) Attempt any TWO: (2x4)**

**08 Marks**

- a) Draw the circuit diagram of weighted resistors method of D-A converter and describe its working.
- b) Draw the logical circuit of serial-in serial-out shift register. Explain with Truth table.
- c)
  - i) Describe the significance of Preset& Clear terminal in J-K flip flop
  - iii) Convert S-R flip flop into D- flip flop and explain the working.

## Sample Question Paper

Course Name : Computer Engineering Group

Course Code : CO/CM/CD/IF/CW

Semester : Third

Subject Title : Digital Techniques

Marks : 100

# 17333

Hours: 3 Hrs.

---

**Q.1) (A) Attempt any SIX.**

**12 Marks**

- a) Define with respect to digital ICs
  - i) Propagation delay
  - ii) Noise immunity
- b) What is positive logic with respect to a digital signal?
- c) Draw the logical symbol, Truth table, and logical expression of AND gate.
- d) State any four Boolean Laws.
- e) Solve the following:
  - i)  $(110101)_2 + (101101)_2$
  - ii)  $(1010)_2 - (1000)_2$  using 1's complement method.
- f) Draw the symbol, logical expression and truth table of 3i/p OR gate.
- g) Draw the truth table of digital comparator IC 7485.
- h) Define the following with respect to DAC
  - i) Resolution
  - ii) Settling time.

**Q.1) (B) Attempt any TWO.**

**08 Marks**

- a) Convert the following
  - i)  $(212)_{10} = (?)_2$
  - ii)  $(11010)_2 = (?)_{10}$
  - iii)  $(436)_8 = (?)_2$
  - iv)  $(206)_8 = (?)_H$
- b) State and prove De Morgan's theorem.
- c) Perform the following BCD arithmetic.
  - i)  $(247)_{10} + (463)_{10}$
  - ii)  $(42)_{10} - (27)_{10}$

**Q.2) Attempt any FOUR:**

**16 Marks**

- a) Implement AND & OR gates using NAND gates only.

b) Given  $Y = \overline{A\overline{B}} + \overline{B\overline{C}} + \overline{A\overline{C}}$

Implement the logical expression using gates.

- c) Perform the following binary operation
  - i)  $11010 \times 1011$
  - ii)  $11011 \div 110$
- d) Design a Half Adder Circuit.
- e) Minimize the following Boolean expression using K – map.

$Y = \sum m_1, m_3, m_5, m_7, m_{10}, m_{11}, m_{14}, m_{15}$ . Draw the logical circuit diagram of minimized expression using basic gates

- f) Draw the block diagram of Decimal to BCD encoder IC 74147 and describe its working with truth table.

**Q.3) Attempt any FOUR:**

**16 Marks**

- a) Simplify the following Boolean Expression using Boolean laws.

i)  $Y = \overline{A}B + ABD + ABCD + BC$

ii)  $Y = \overline{A} + \overline{A}B + \overline{A}B\overline{C} + \overline{A}\overline{B}CD$

- b) Draw the logical block diagram of 4:1 multiplexers and describe its working. Give the expression for the output and draw the circuit diagram using gates.

- c) Given K-map

	$\overline{C}\overline{D}$	$\overline{C}D$	$CD$	$C\overline{D}$
$\overline{A}\overline{B}$	0	0	1	0
$\overline{A}B$	1	1	1	1
$AB$	0	1	1	1
$A\overline{B}$	0	0	1	0

Write the minimized logical expression and draw the logical circuit using universal gates.

- d) Standardize the following Boolean expression

i)  $Y = AB + \overline{B}C + A\overline{C}$

ii)  $Y = (A+C). (B+\overline{C}) + (\overline{A}+B)$

- e) Draw the logical circuit diagram of clocked SR flip flop using NAND gates and describe its working with truth table.

- f) Draw the logical circuit diagram of a 3 bit asynchronous UP Counter. Describe its working with timing diagram.


**Q.4) Attempt any FOUR:**

**16 Marks**

- a) What is modulus of a counter? Show the method to determine the number of flip flops for a mod - 46 Counter?

- b) Give 2 advantages and 2 disadvantages of A - D Converters.

 - c) Prepare the truth table for the given logical Circuit diagram and from the truth table identify the flip flop.



- d) Explain the significance of Preset & Clear terminals with truth table of JK Flip flop.
- e) Classify memories. What are the mechanisms used for erasing EPROM.
- f) Draw the block diagram of successive approximation method of A-D Converter & describe its working.

**Q.5) Attempt any FOUR:**


**16 Marks**

- a) Perform the following Subtraction using 2's complement method.
  - i)  $1000 - 01001$
  - ii)  $11100 - 00011$
- b) Draw the block diagram of Sequential logic and state the importance of clock signal in it.
- c) Given logical equation  
 $Y = (A+BC)(B+\bar{C}A)$   
 Design a circuit using basic gates to realize this function.
- d) Draw the circuit of a ring counter and describe with timing diagram.
- e) Draw the block diagram of BCD – 7 segment decoder / driver. Describe its working.
- f) Draw the logical circuit diagram of PISO shift register. Describe its working.

**Q.6) Attempt any TWO:**

**16 Marks**

 - a) i) State the applications of de multiplexers. (2 Marks)
- ii) Design 16:1 multiplexer using 4:1 multiplexers only. (6 Marks)
- b) i) Determine the output of the following figures and shows that  $Y_1 = Y_2$ . (2 marks)



- ii) State two applications of shift registers. (2 marks)
- iii) Draw a mod 5 asynchronous counter. Explain in brief. (4 marks)
- c) i) Draw the Circuit diagram of R – 2R Ladder method of D – A Converter and describe its working. (4 Marks)
- ii) A D/A converter has a full scale analog o/p of 10 V and accepts 4 binary bits as inputs. Find the Voltage Corresponding to each analog step. (4 marks)